 


## Hardware testing and design for testability



## A Digital System requires testing before and after it is manufactured

- **Level 1:** behavioral modeling and test benches
  - Check for correct design and algorithms
- **Level 2:** logic level testing
  - Check for correct logic and whether the design meets specifications
- **Level 3:** circuit level testing
  - Check for correct implementation and whether the timing is correct
- **Level 4:** post-manufacture testing
  - Check for defects

- **Digital systems should be designed so that they are easy to test**
- **Important to develop efficient testing methods**
  - **Design for testability (DFT)**
  - **Automatic test pattern generators (ATPG)**
  - **Built in Self Test (BST)**
- **Testing Combinational Logic**
- **Testing Sequential Logic**
- **Scan Testing**
- **Boundary Scan**


## Testing Combinational Logic

- **Stuck-at-1 (s-a-1) and Stuck-at-0 (s-a-0)**
  - if the input to a gate is *shorted to ground*, it is **s-a-0**
  - if the input to a gate is *shorted to positive power supply*, it is **s-a-1**
  - if the input to a gate is an *open circuit*, it may act as **s-a-0** or **s-a-1**
- **For s-a-0, provide '1' as input**
  - To check if it will flip '1' to '0'
- **For s-a-1, provide '0' as input**
  - To check if it will flip '0' to '1'


- Finding AND and OR Gate Stuck-at-faults

If s-a-0 AND gate will produce 0

s-a-0

 


(a)

 


(b)

s-a-1

s-a-1

 

(c)

 


(d)

s-a-0


## Two-level circuit

**s-a-0**

 


a	b	c	d	e	f	g	h	i	Faults Tested
1	1	1	0	X	X	0	X	X	a0, b0, c0, p0
0	X	X	1	1	1	0	X	X	d0, e0, f0, q0
0	X	X	0	X	X	1	1	1	g0, h0, i0, r0
0	1	1	0	1	1	0	1	1	a1, d1, g1, p1, q1, r1
1	0	1	1	0	1	1	0	1	b1, e1, h1, p1, q1, r1
1	1	0	1	1	0	1	1	0	c1, f1, i1, p1, q1, r1

**s-a-1**

 

We have no clue about the internal faults, we can provide inputs and look at outputs: the fault will propagate by setting specific pins to 1 or 0

## Multi-level circuit

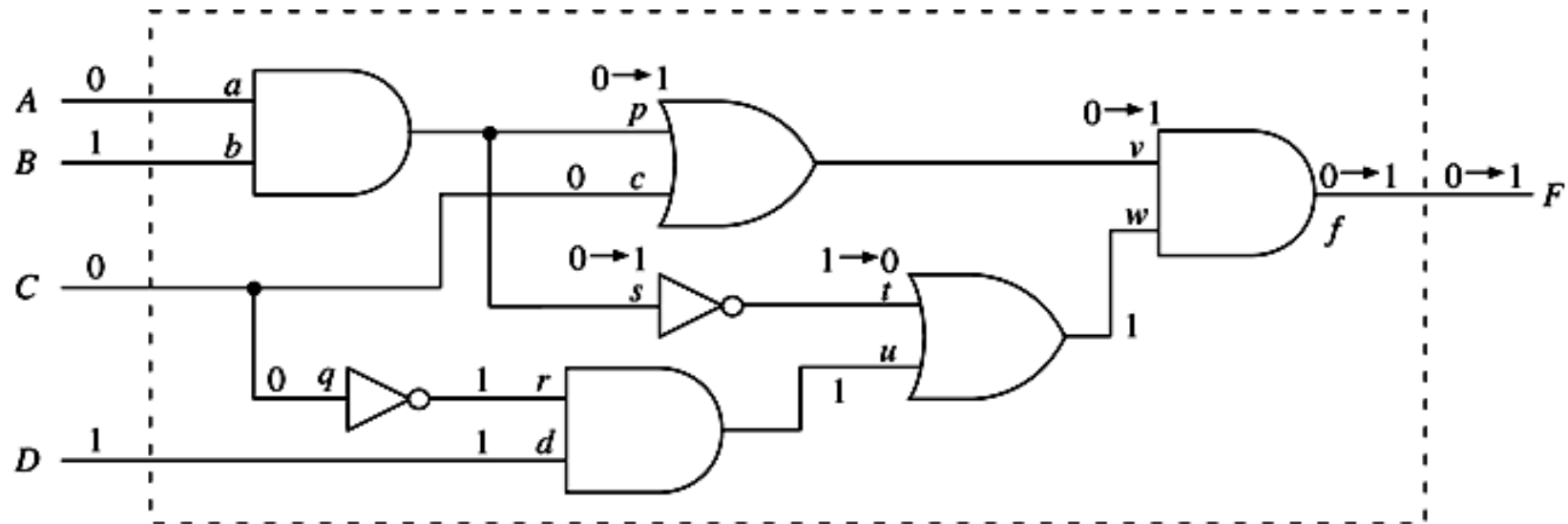

Test Vectors				Normal Gate Inputs												Faults Tested														
A	B	C	D	a	b	p	c	q	r	d	s	t	u	v	w	F														
0	1	0	1	0	1	0	0	0	1	1	0	1	1	0	1	0	0	a1	p1	c1	v1	f1								
1	1	0	1	1	1	1	0	0	1	1	1	0	1	1	1	1	1	a0	b0	p0	q1	r0	d0	u0	v0	w0	f0			
1	0	1	1	1	0	0	1	1	0	1	0	1	0	1	1	1	1	b1	c0	s1	t0	v0	w0	f0						
1	1	0	0	1	1	1	0	0	1	0	1	0	0	1	0	0	0	a0	b0	d1	s0	t1	u1	w1	f1					
1	1	1	1	1	1	1	1	1	0	1	1	0	0	1	0	0	0	a0	b0	q0	r1	s0	t1	u1	w1	f1				




- **Bridging fault occurs when two unconnected signal lines are shorted**
- Finding a minimum set of test vectors that will test all possible faults is very difficult
  - Use small set of testing vectors that can test most faults
  - Use algorithms and programs that will generate set of test vectors
 
## Testing Sequential Logic

- **Testing Sequential Logic is more difficult than combinational logic**
  - Sequence of inputs and resulting outputs
  - No access to state of flipflops
  - Very large number of tests are required
  - Use a small set of test sequences that can be adequate

- Look for all possible state transitions and outputs



**X=010110011**


**Z=001111100**

**(both solid and dashed)**

Q1Q2	State	Next State		Output	
		X = 0	1	X = 0	1
00	S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	0	0
10	S <sub>1</sub>	S <sub>0</sub>	S <sub>2</sub>	1	1
01	S <sub>2</sub>	S <sub>3</sub>	S <sub>3</sub>	1	1
11	S <sub>3</sub>	S <sub>2</sub>	S <sub>0</sub>	1	0
 
## Find the distinguishing sequence

- Two states are distinguishable if an input sequence produces different output sequences
- In this example, **11** is the distinguishing sequence



Q1Q2	State	Next State		Output	
		X = 0	1	X = 0	1
00	S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	0	0
10	S <sub>1</sub>	S <sub>0</sub>	S <sub>2</sub>	1	1
01	S <sub>2</sub>	S <sub>3</sub>	S <sub>3</sub>	1	1
11	S <sub>3</sub>	S <sub>2</sub>	S <sub>0</sub>	1	0


## How to find distinguishing sequence?

1) Apply 1 to all states and see which states produce identical outputs

**1** → {S<sub>0</sub>, S<sub>3</sub>} → **0** and **1** → {S<sub>1</sub>, S<sub>2</sub>} → **1**

2) Apply 1 again to find distinct states within each group

 **11** → S<sub>0</sub> → **01**, **11** → S<sub>3</sub> → **00**, **11** → S<sub>1</sub> → **11**, **11** → S<sub>2</sub> → **10**




Q1Q2	State	Next State		Output	
		X = 0	1	X = 0	1
00	S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	0	0
10	S <sub>1</sub>	S <sub>0</sub>	S <sub>2</sub>	1	1
01	S <sub>2</sub>	S <sub>3</sub>	S <sub>3</sub>	1	1
11	S <sub>3</sub>	S <sub>2</sub>	S <sub>0</sub>	1	0

Input	Output	Transition Tested
0 1 1	0 0 1	S <sub>0</sub> to S <sub>2</sub>
1 1 1	0 1 1	S <sub>0</sub> to S <sub>3</sub>
1 0 1 1	0 1 0 1	S <sub>1</sub> to S <sub>0</sub>
1 1 1 1	0 1 1 0	S <sub>1</sub> to S <sub>2</sub>
1 1 0 1 1	0 1 1 0 0	S <sub>2</sub> to S <sub>3</sub>
1 1 1 1 1	0 1 1 0 0	S <sub>2</sub> to S <sub>3</sub>
1 1 0 0 1 1	0 1 1 1 1 0	S <sub>3</sub> to S <sub>2</sub>
1 1 0 1 1 1	0 1 1 0 0 1	S <sub>3</sub> to S <sub>0</sub>

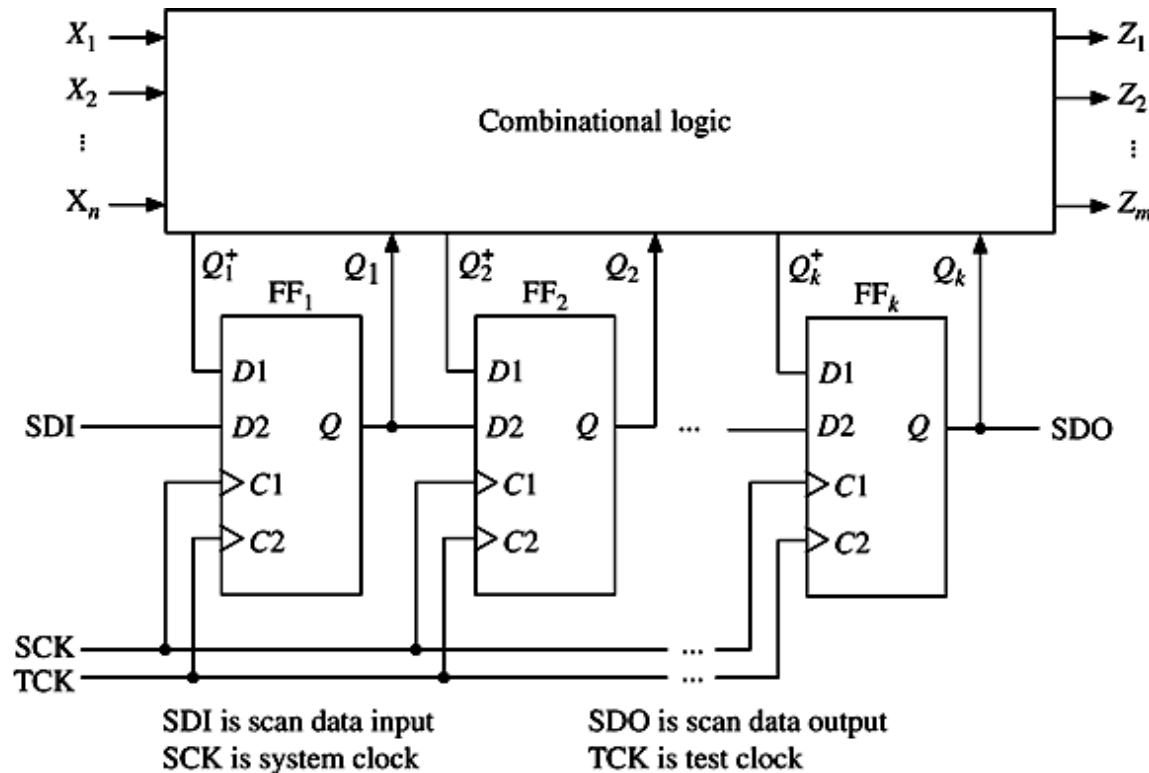
## Scan Testing

- **Instead of observing outputs, observe the state of flip-flops**
- How can we observe the state of all flip-flops without using up a large number of pins on the IC?
  - Create parallel to serial shift-register out of the flipflops and use a single serial output pin






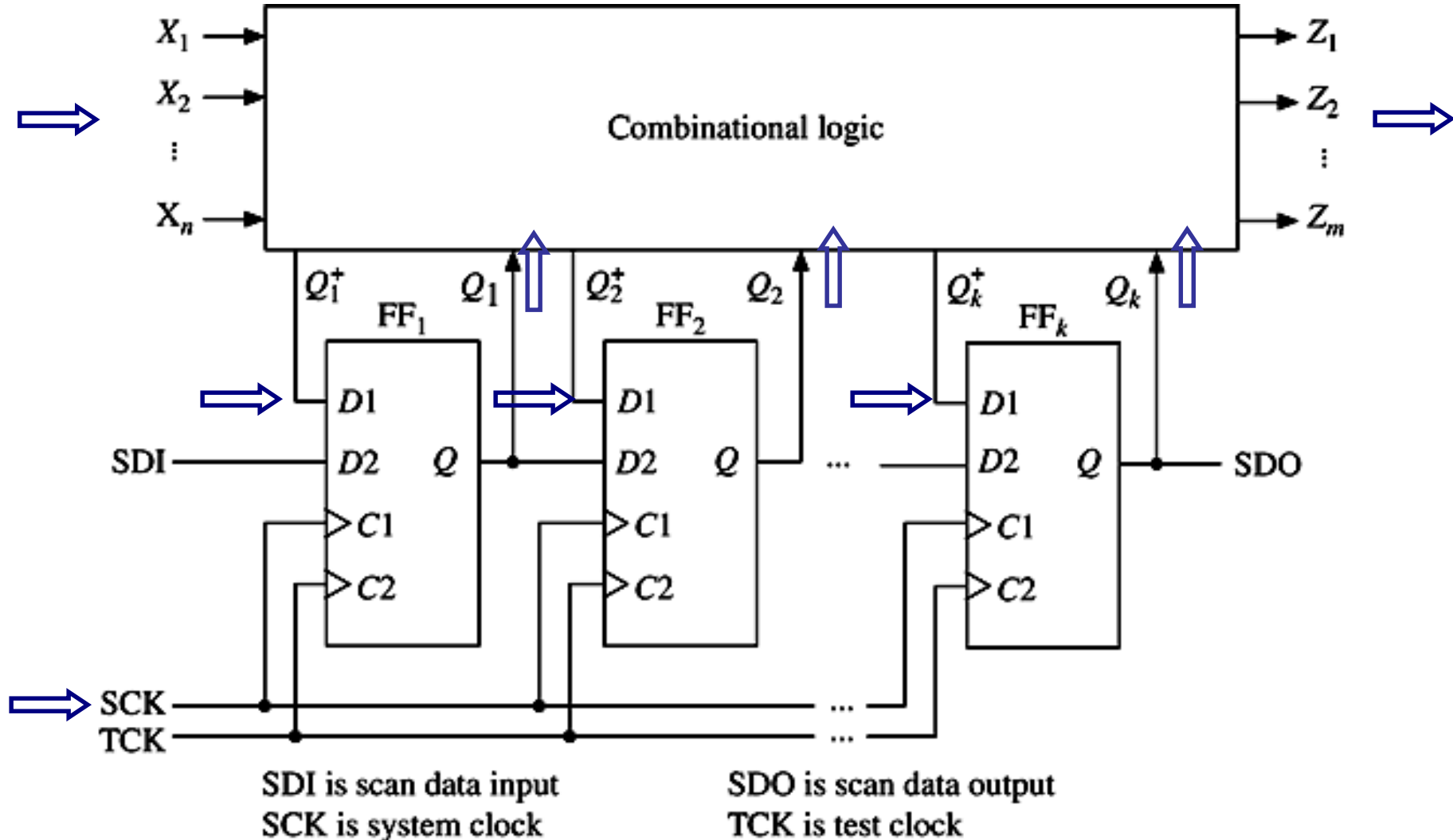
## ■ Scan Path Test Circuit (Normal Operation)



## ■ Scan Path Test Circuit (Test)

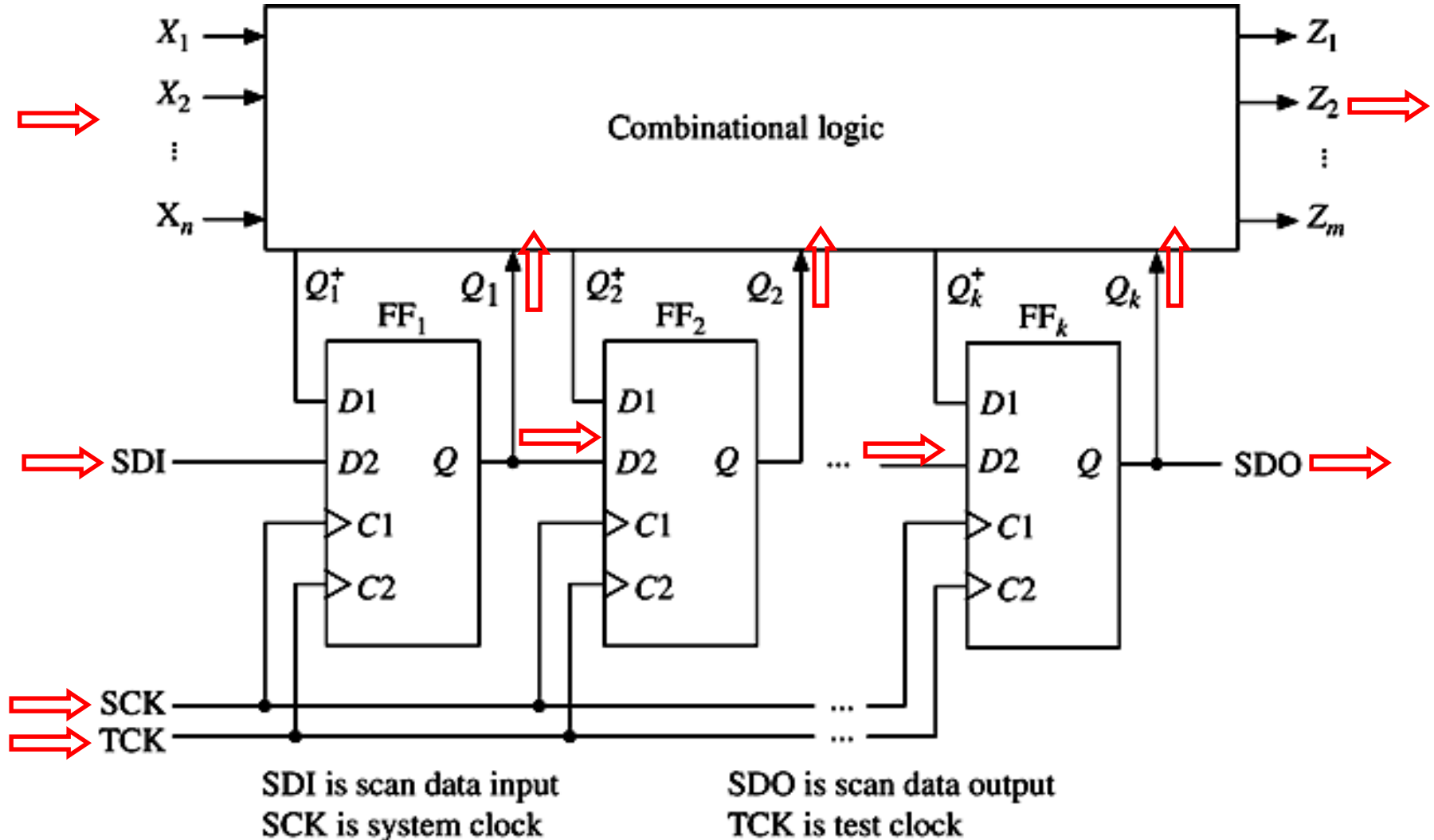


- Scan Path Test Circuit (Test)

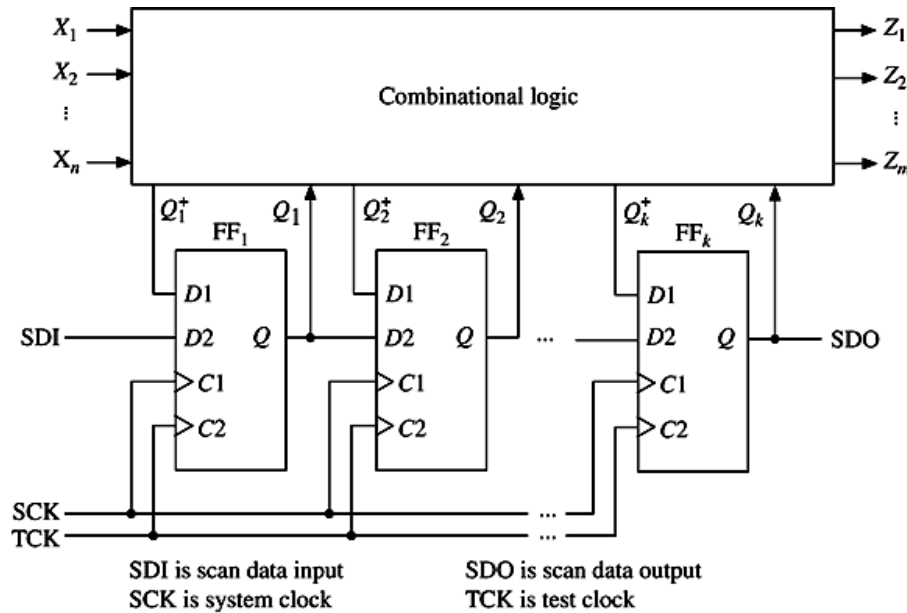

- Scan in the test vector  $Q_i$  values via **SDI** using test clock **TCK**
- Apply the corresponding test values to the  $X_i$  inputs
- Verify output  $Z_i$  values
- Apply one clock pulse **SCK** to store new values of  $Q_i^+$  into the FFs
- Scan and verify  $Q_i$  values by pulsing test clock TCK
- Repeat the above for each test vector

		$Q_1^+Q_2^+Q_3^+$				$Z_1Z_2$			
$Q_1Q_2Q_3$	$X_1X_2=$	00	01	11	10	00	01	11	10
101		010	110	011	111	10	11	00	01

 

\*Read output (output at other times not shown)


- Shift **101** using **TCK** via **SDI**:  $Q_3$  (LSB) First,  $Q_1$  (MSB) last

**Note that 101 is a unique pattern which does not rely on  $X_1$  and  $X_2$**

# Scan Testing: Example

21

		$Q_1^+Q_2^+Q_3^+$				$Z_1Z_2$			
$Q_1Q_2Q_3$	$X_1X_2=$	00	01	11	10	00	01	11	10
101		010	110	011	111	10	11	00	01

 

\*Read output (output at other times not shown)


- Apply input  $X_1X_2=00$ , verify that  $Z_1Z_2=10$



**\*Read output (output at other times not shown)**

- Suketu Naik**

		$Q_1^+Q_2^+Q_3^+$				$Z_1Z_2$			
$Q_1Q_2Q_3$	$X_1X_2=$	00	01	11	10	00	01	11	10
101		010	110	011	111	10	11	00	01

 

\*Read output (output at other times not shown)

- Shift **101** using **TCK** via **SDI**:  $Q_3$  (LSB) First,  $Q_1$  (MSB) last


**Note that 101 is a unique pattern which does not rely on  $X_1$  and  $X_2$**



# Scan Testing: Example

25


		$Q_1^+Q_2^+Q_3^+$				$Z_1Z_2$			
$Q_1Q_2Q_3$	$X_1X_2=$	00	01	11	10	00	01	11	10
101		010	110	011	111	10	11	00	01

 

\*Read output (output at other times not shown)

- Apply input  $X_1X_2=01$ , verify that  $Z_1Z_2=11$


		$Q_1^+Q_2^+Q_3^+$				$Z_1Z_2$			
$Q_1Q_2Q_3$	$X_1X_2=$	00	01	11	10	00	01	11	10
101		010	110	011	111	10	11	00	01

 

\*Read output (output at other times not shown)

- Single pulse on **SCK** to advance circuit to state **110**

		$Q_1^+Q_2^+Q_3^+$				$Z_1Z_2$			
$Q_1Q_2Q_3$	$X_1X_2=$	00	01	11	10	00	01	11	10
101		010	110	011	111	10	11	00	01

 


\*Read output (output at other times not shown)


- Verify that **SDO** shows the previous state **010**

Continue to the next state ...

 - Replace flip-flops with two-port flip-flops
- **Connect them together in a chain and create Scan chain (shift register)**




(a) Without scan chain

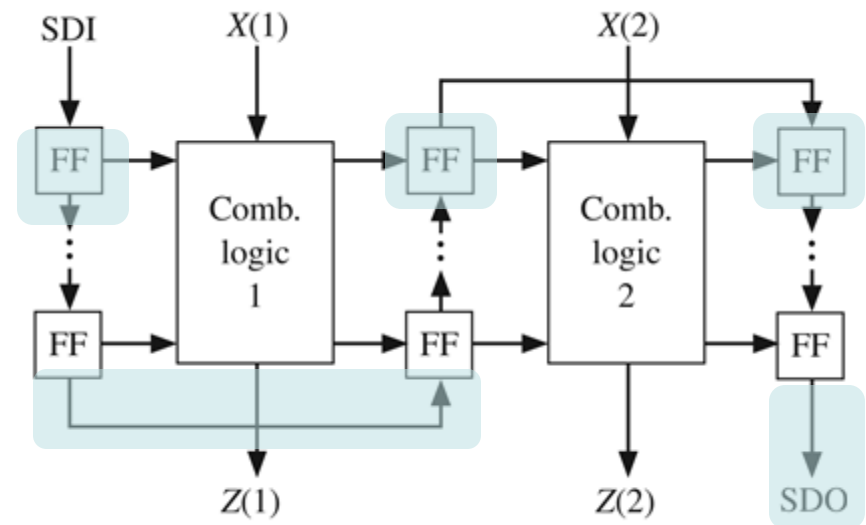

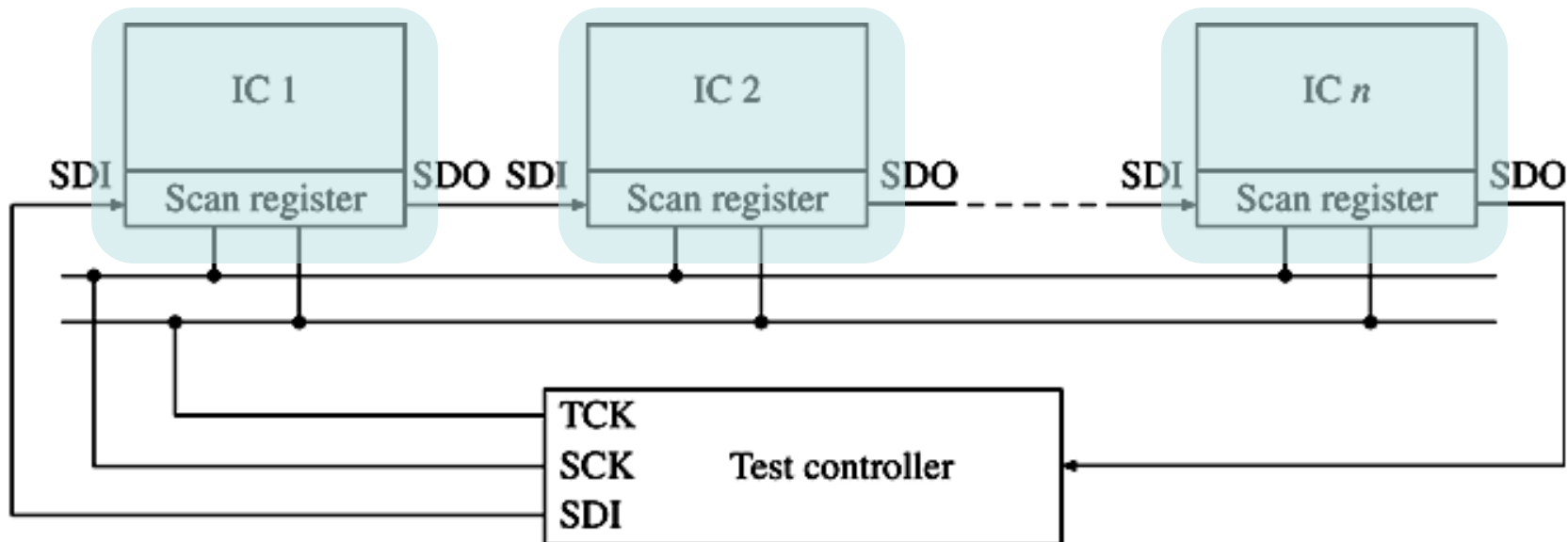
(b) With scan chain added

- Chain scan registers together
- **The whole PCB can be scanned using single serial port**





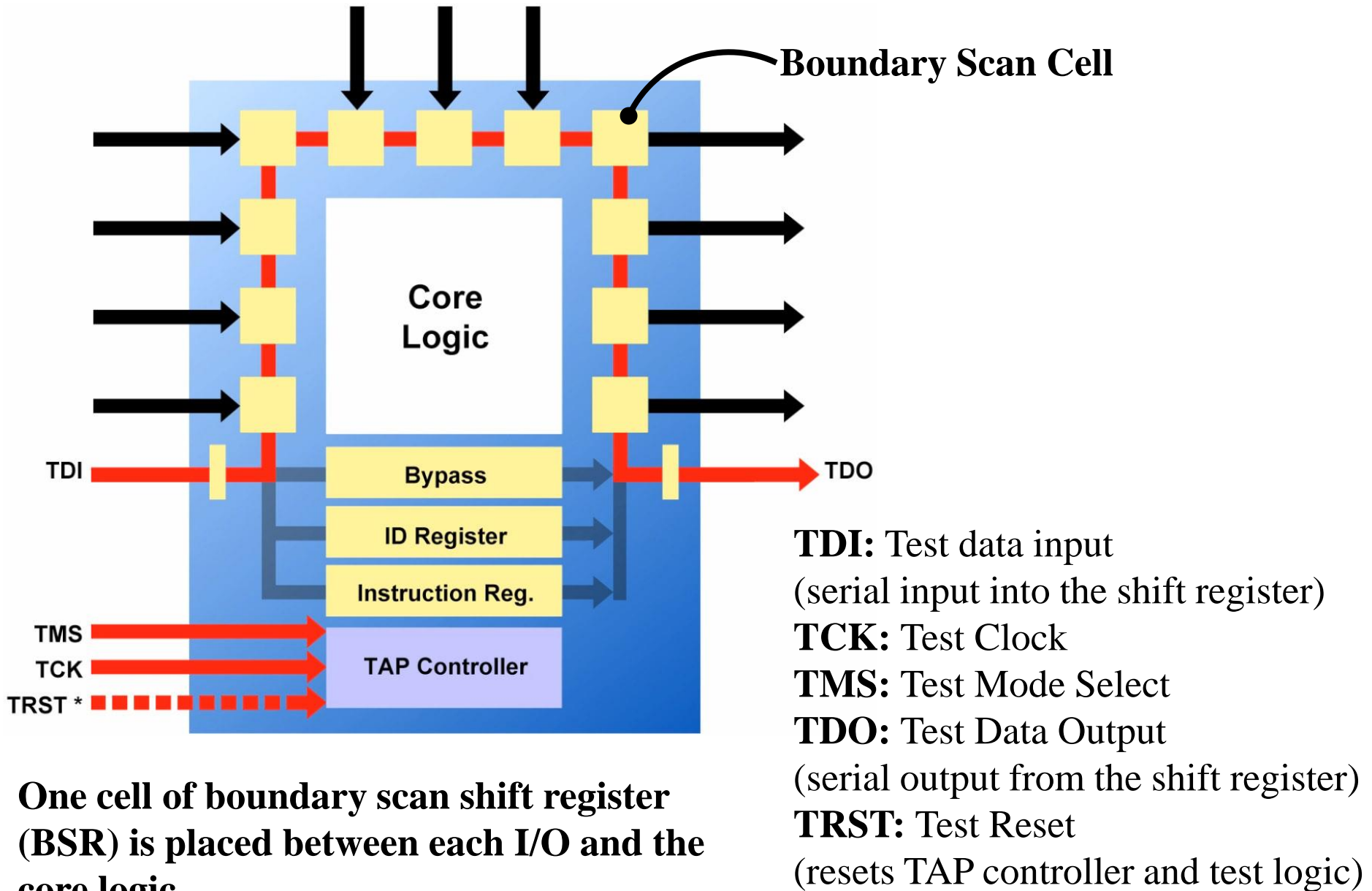
## Boundary Scan


- **Boundary Scan was developed to test a complex PCB with many ICs**
- **JTAG (Joint Test Action Group)** developed the standard for boundary scan
  - Standard Test Access Port and Boundary-Scan Architecture
  - **Multiple ICs can be linked together on PCB and tested using few pins on the edge**






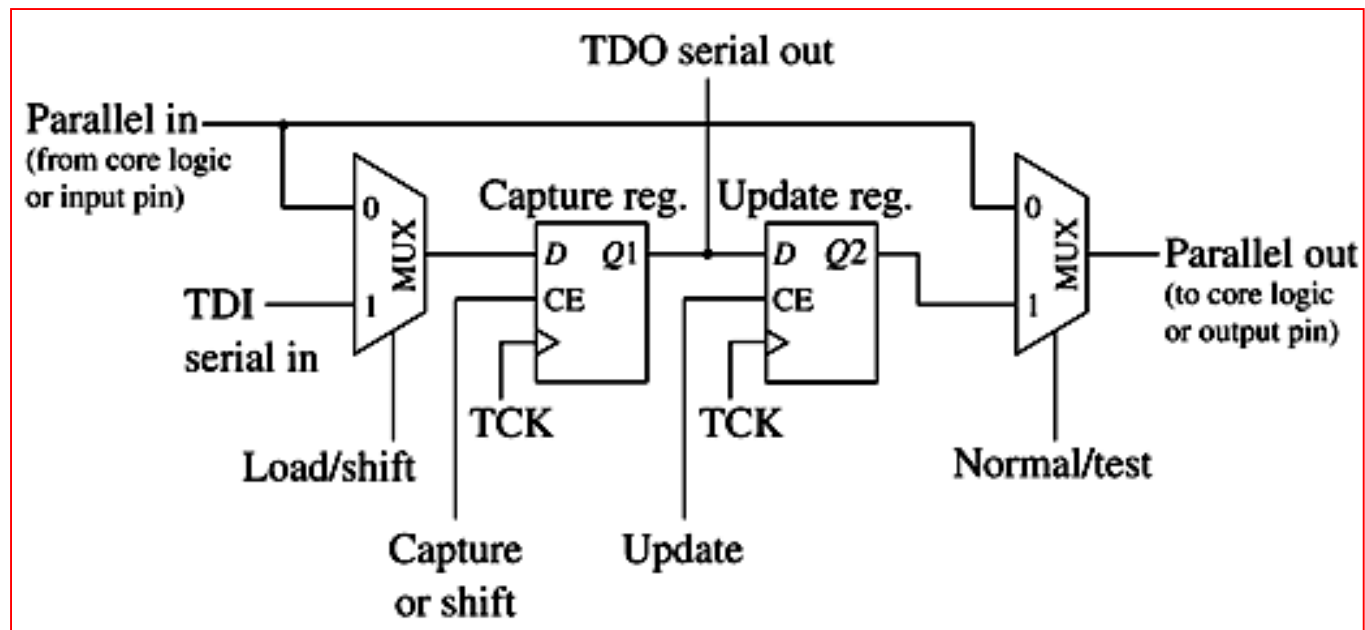 

 

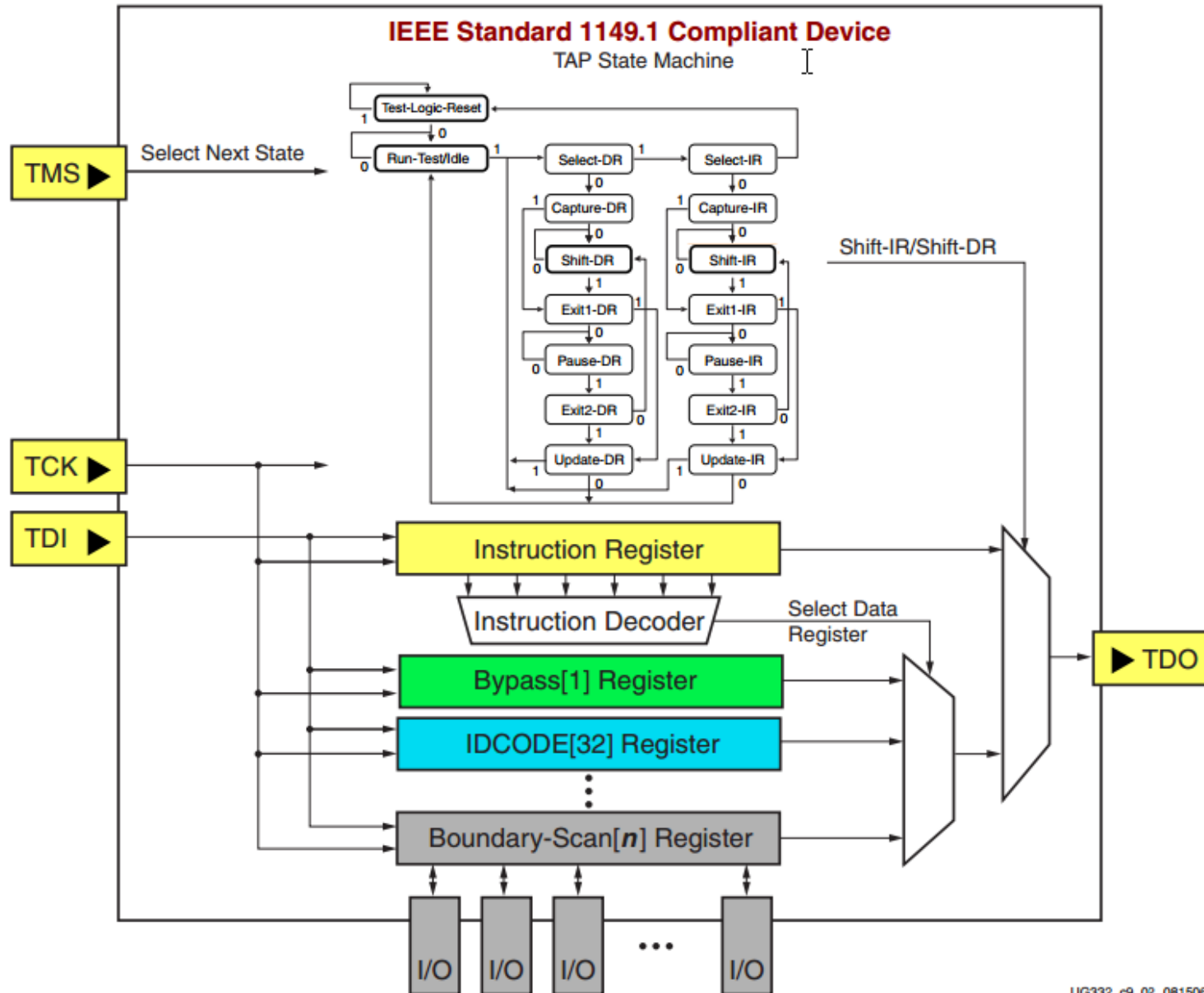

UG332\_c9\_02\_081506

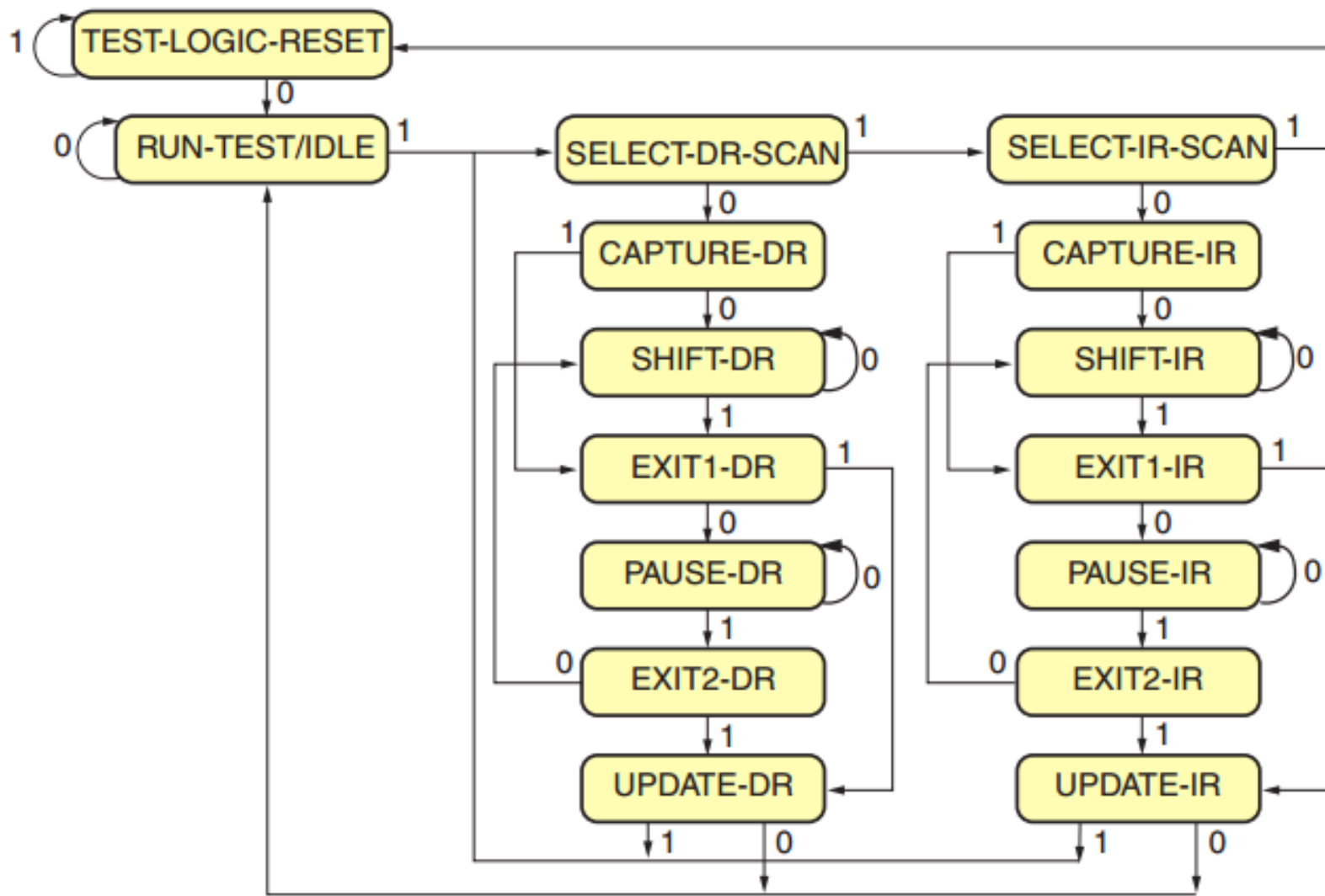

UG332\_C9\_03\_080906

 


Figure 12-15: Attaching a JTAG Parallel Programming Cable to the Board

Table 12-2: Cable Connections to J12 Header

Cable and Labels	Connections					
J12 Header Label	SEL	SDI	SDO	SCK	GND	VCC
JTAG3 Cable Label	TMS	TDI	TDO	TCK	GND	VCC
Flying Leads Label	TMS/ PROG	TDI/ DIN	TDO/ DONE	TCK/ CCLK	GND/ GND	VREF/ VREF

Does this look familiar?

